


## Lecture 4 (F-I ch23, W: 32, 33)

### The RLC circuit

A Reminder : There are 3 basic circuit elements:

The Capacitor made, for example, out of 2 parallel metallic plates separated by small distance filled with an insulator.

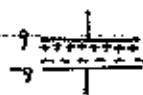
Its basic property is the linear relation between the voltage difference  $V$  between the plates and the charge  $+q$  and  $-q$  on them:



$$V = \frac{q}{C} \quad C: \text{the capacitance of the capacitor}$$

The Resistor resist the flow of electrical current like metallic wires.

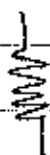
Basic property: (Ohm's law) linear relation between the voltage drop  $V$  across the resistor and the current  $I$  through it:



$$V = RI = R \frac{dq}{dt} \quad R: \text{the Resistance}$$


The Inductor : A Coil When you drive current through a coil a magnetic field develops.  
A changing current causes a change in flux

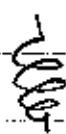magnetic field and this by Faraday's induction law induces a voltage drop across the coil's ends.



Basic property  $V = L \frac{dI}{dt} = L \frac{d^2q}{dt^2}$   $L$ : the Self Inductance

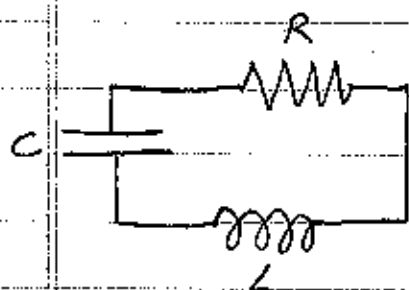Now build a closed circuit out of these 3 elements



Since there are no voltage generators in this circuit the sum of the voltage drops across the 3 elements must vanish:

$$V_L + V_R + V_C = 0$$

$$\Rightarrow L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$


Note that by writing this equation as

~~$$\frac{q}{C} + R \frac{dq}{dt} = -L \frac{d^2q}{dt^2}$$~~

$$L \frac{d^2q}{dt^2} = -\frac{1}{C}q - R \frac{dq}{dt}$$

and interpreting  $q(t)$  as a coordinate  $x(t)$  of a mechanical object we can treat it as per Newton's second law for the mechanical object
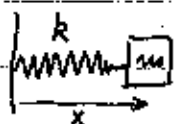
$$m \frac{d^2x}{dt^2} = F = -\underbrace{kx}_{\text{spring restoring force}} - \underbrace{\gamma \frac{dx}{dt}}_{\text{friction force proportional to the velocity}}$$



• spring restoring force  
friction force proportional to the velocity.

If we identify:

	<u>Mechanical Property</u>		<u>Electrical Property</u>
dep. variable	$x(t)$	- position	$q(t)$ - charge
inertia	$m$	- mass	$L$ - inductance
resistance	$\delta$	- drag coeff.	$R$ - resistance
stiffness	$k$	- spring const.	$\frac{1}{C}$ - inverse capacitance

Let us now solve the equation using the complex numbers method:

Insert  $q = e^{i\omega t}$  to the equation

$$\Rightarrow \left[ -\omega^2 + \frac{R}{L}i\omega + \frac{1}{LC} \right] e^{i\omega t} = 0$$

Have a non trivial solution if  $\omega^2 - \frac{iR}{L}\omega - \frac{1}{LC} = 0$

A quadratic equation with solutions -

$$\omega_{\pm} = \frac{-\left(-\frac{iR}{L}\right) \pm \sqrt{\left(-\frac{iR}{L}\right)^2 - 4\left(-\frac{1}{LC}\right)}}{2}$$

$$\Rightarrow \omega_{\pm} = \frac{iR}{2L} \pm \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

The general solution is then  $\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$

$$q(t) = A_+ e^{-\frac{R}{2L}t} e^{i\omega t} + A_- e^{-\frac{R}{2L}t} e^{-i\omega t}$$


$$= e^{-\frac{R}{2L}t} \left[ A_+ e^{i\omega t} + A_- e^{-i\omega t} \right]$$

~~can produce an oscillating part just as in the particular~~

We thus find that  $R$  causes the damping of the oscillations.


Depending on the parameters we can have different behaviours:

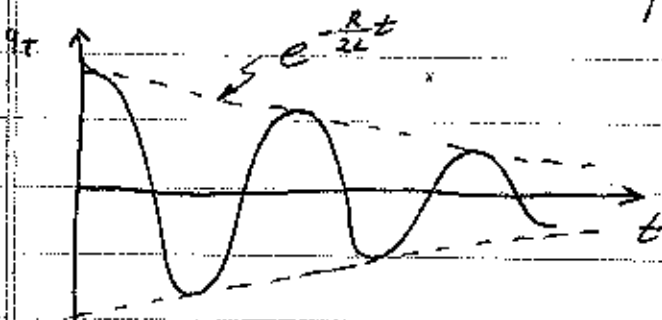I. For  $\frac{1}{LC} > \frac{R^2}{4L^2} \rightarrow \omega'$  is real and the expression in brackets for  $q$  produces oscillatory behavior just as in the pendulum case



damped oscillations with period  $\omega'$

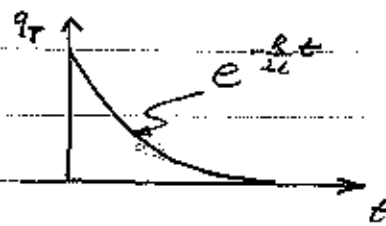II.  $\frac{1}{LC} = \frac{R^2}{4L^2} \rightarrow \omega' = 0$



critically damped

III.  $\frac{1}{LC} < \frac{R^2}{4L^2} \rightarrow \omega'$  is imaginary  $\omega' = i\omega''$   $\omega'' = \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$

$$q_T = e^{-\frac{R}{2L}t} \left[ A_+ e^{-\omega''t} + A_- e^{\omega''t} \right]$$

this term decays faster

The current decays like  $e^{-\left(\frac{R}{2L} - \omega''\right)t}$ ; more slowly than the critically damped case it's called "overdamped".

