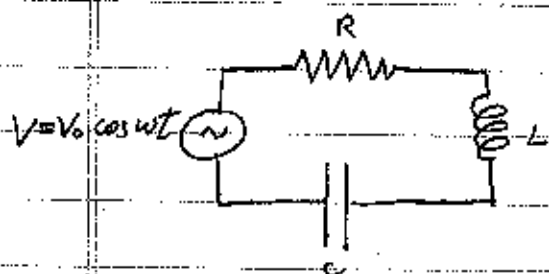


Lecture 5 + demonstration: forced harmonic oscillator

Now let's add a voltage generator to the circuit



The equation now reads $L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = V = V_0 \cos \omega t$

We will now treat V as well as q as complex quantity

Writing $q = q_r + i q_i$, $V = V_r + i V_i$ get

$$\left[L \frac{dq_r}{dt^2} + R \frac{dq_r}{dt} + \frac{q_r}{C} \right] + i \left[L \frac{dq_i}{dt^2} + R \frac{dq_i}{dt} + \frac{q_i}{C} \right] = V_r + i V_i$$

→ Thus if we take $V = V_0 e^{i\omega t}$ the real part of q satisfies the equation satisfied by the real physical quantities.

Put now $q = A e^{i\omega t}$ to get

$$\left[L(i\omega)^2 + R(i\omega) + \frac{1}{C} \right] A e^{i\omega t} = V_0 e^{i\omega t}$$

$$\Rightarrow A = \frac{V_0}{L(\omega_0^2 - \omega^2) + iR\omega} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

Can write $\frac{A}{V_0}$ as $\rho e^{i\theta}$ in the following way


$$\frac{A}{V_0} = \frac{L(\omega_0^2 - \omega^2) - iR\omega}{[L(\omega_0^2 - \omega^2) + iR\omega][L(\omega_0^2 - \omega^2) - iR\omega]}$$

$$= \frac{L(\omega_0^2 - \omega^2) - iR\omega}{L^2(\omega_0^2 - \omega^2)^2 + (R\omega)^2}$$

$$\Rightarrow \rho^2 = \frac{L^2(\omega_0^2 - \omega^2)^2 + (R\omega)^2}{[L^2(\omega_0^2 - \omega^2)^2 + (R\omega)^2]^2} = \frac{1}{L^2(\omega_0^2 - \omega^2)^2 + (R\omega)^2} = \left[\frac{\text{Re } \frac{A}{V_0}}{\left(\frac{\text{Im } \frac{A}{V_0}}{\rho} \right)^2} \right]^2$$


$$\tan \theta = -\frac{R\omega}{L(\omega_0^2 - \omega^2)} = \left[\frac{\text{Im } \frac{A/V_0}{\rho}}{\text{Re } \frac{A/V_0}{\rho}} \right]$$
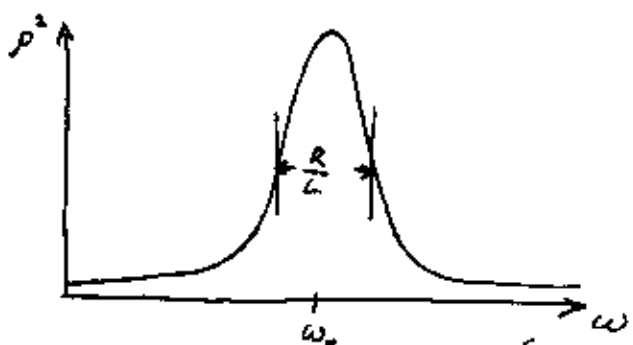
$$\Rightarrow q = V_0 \rho e^{i(\omega t + \theta)}$$



The Quality factor: $Q = \frac{\text{resonance frequency}}{\text{width of resonance}}$

$$= \frac{\omega_0 L}{R}$$

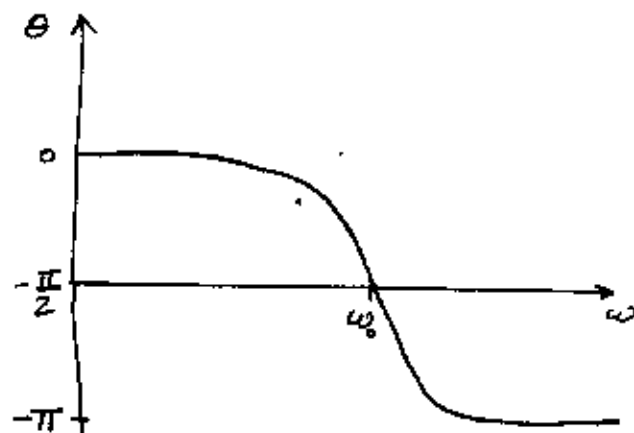

* The response of the system is peaked ~~for~~ when the ~~ext~~ frequency of the external perturbation matches the natural frequency ω_0 of the system: the frequency it has without external force or dissipation.

